

4. Take the _____ wire and plug one end into _____ and leave the other end hanging.
 - a. Plug one end of the _____ wire into _____ and leave the other end hanging.
 - b. Plug one end of the _____ wire into _____ and leave the other end hanging.
5. Take the long (_____) wire and plug it into any pin in the _____ column on the right side of the breadboard. Leave the other end hanging.

